

## **Lab Report #7**

Hanz Chua U26738740

Viraj Amarasinghe U14806439

Jian Gong U42910460

### **Introduction**

The purpose of this lab was to help us gain a deeper understanding of sequential circuit design, and in particular, counters. We designed and implemented a 3-bit gray code counter using JKFFs.

### **Methods and Materials**

Wires

Breadboard

2 JK Flip Flop ICs

2 AND Gate ICs

1 OR Gate IC

3 LED

3 Resistors

Push Button

In this lab, we designed a gray code counter. We began with drawing the state transition diagram and next state table for the gray code counter. We designed the circuit and implemented it using JK flip flops, since we did not have D or T flip flops. We set up the function generator to produce a 1 Hz square wave. We made the signal slow enough so we could see the changing states using LEDs. We then implemented the circuit and tested its functionality

### **Results**

We observed that the gray code counter circuit worked as planned; When we pressed the button the LEDs lit up to the corresponding number and sequence associated with the gray code order. We also observed that we can also observe the output after connecting the circuit to a 7-segment display rather than the LEDs. After resolving some issues/mistakes, we concluded that the results came out as expected and contributed to the goal of the experiment; to help us gain a deeper understanding of sequential circuit design and counters.

### **Conclusion**

In conclusion, when someone presses the button on our circuit, the counter counts up and the output, whether it is an LED or 7 segment display, updates to the corresponding state. Issues we ran into included omitting resistors, burning out LEDs and even a display, and plugging in wires to wrong holes.

## Questions

### 1. Verilog testbench, module, and EPWave

#### Testbench

```
module testbench();
    reg clock, reset;
    reg [2:0] currentState;
    wire [2:0] nextState;

    gray_counter counter(clock, reset, currentState, nextState);

    initial begin
        clock = 0;
        reset = 1;
        forever #5 clock = ~clock;
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;

        #10 reset = 0;
        currentState = 3'b000;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);
        currentState = nextState;

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);
    end
endmodule
```

```

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        #10 currentState = nextState;
        $monitor("Clock: %b, Current state = %b, Next state = %b\n",
clock, currentState, nextState);

        $finish;
    end
Endmodule

```


### Module

```


module gray_counter(clock, reset, currentState, nextState);
    input clock, reset;
    input reg [2:0] currentState;
    output reg[2:0] nextState;
    always @(posedge clock) begin
        if (reset) begin
            nextState <= 3'b000;
        end
        else begin
            case(currentState)
                (3'b000) : nextState <= 3'b001;
                (3'b001) : nextState <= 3'b011;
                (3'b011) : nextState <= 3'b010;
                (3'b010) : nextState <= 3'b110;
                (3'b110) : nextState <= 3'b111;
                (3'b111) : nextState <= 3'b101;
                (3'b101) : nextState <= 3'b100;
                (3'b100) : nextState <= 3'b000;
            endcase
        end
    end
end
endmodule

```

## EPWave

 
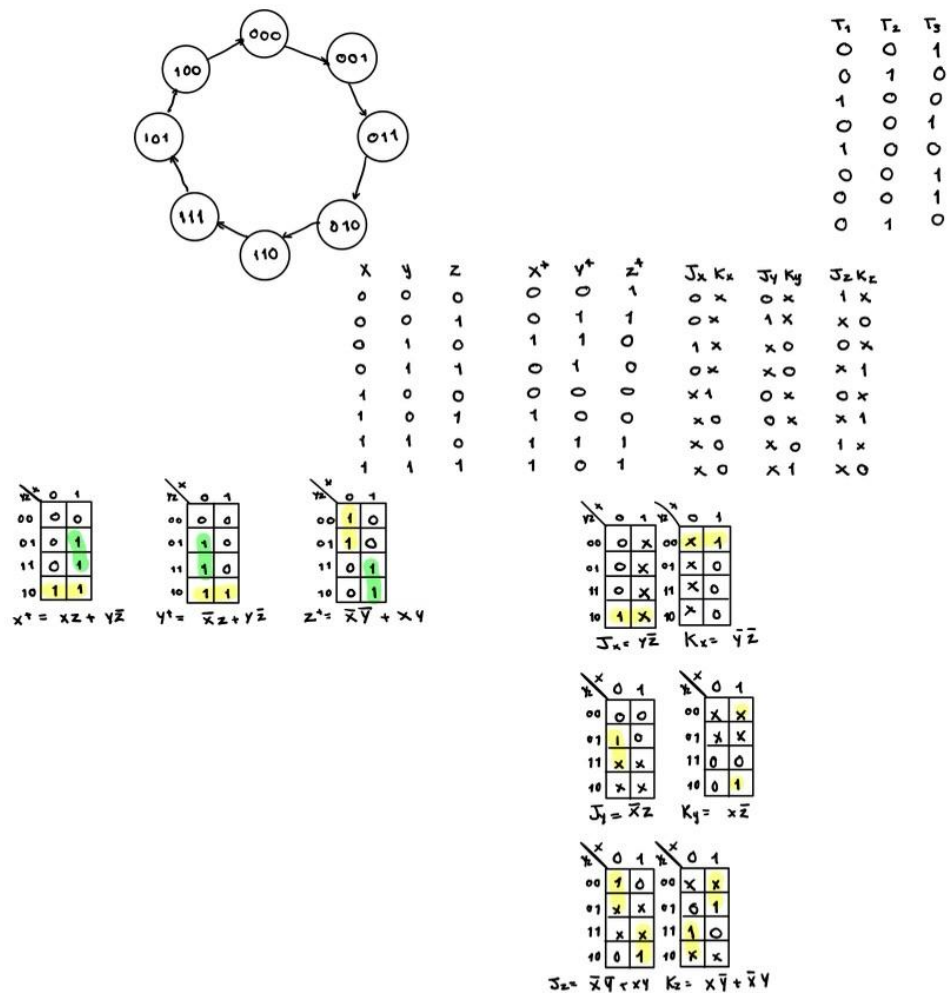
## 2. State transition diagram, truth tables, and K-Maps



### 3. Circuit Diagrams

